

Revision 1. - Electricity

1. Case 1.

$$P = 50W$$

$$V = 220V$$

$$P = \frac{V^2}{R}$$

$$\therefore 50 = \frac{220 \times 220}{R}$$

$$R = \frac{220 \times 220}{50} \Rightarrow \frac{48400}{50}$$

$$\therefore R_1 = \underline{\underline{968 \Omega}}$$

Case 2.

$$P = 25W$$

$$V = 220V$$

$$P = \frac{V^2}{R}$$

$$\Rightarrow 25 = \frac{220 \times 220}{R}$$

$$R = \frac{48400}{25} \Rightarrow 19360$$

$$\therefore R_2 = 19360 \Omega$$

$$\text{as } R_2 > R_1$$

$$R_2 - R_1 = 19360 - 9688$$

$$= \underline{\underline{18368 \Omega}}$$

\therefore The bulb with 25W, 220V

has higher resistance and by 18368 Ω than the bulb of 50W, 220V

2.

$$R_1 = \frac{\rho l}{A_1}$$

$$\text{ratio} = \frac{\rho l}{A}$$

$$R_2 = \frac{\rho l}{A_2}$$

$$= \frac{1}{1} \Rightarrow \underline{\underline{1:1}}$$

22
22
44
44
484
x 22
5) 4840
45
34
30
44
20
40
x 96880
5) 48400
45
34
30
44
20
40
x 193376
5) 966880
5
46
45
16
15
48
15
38
35
30

193376
9688
9 12 16 16
193376
- 9688
183688

3. (i) (c) a milliammeter, a resistor and a voltmeter ✓


(ii) (a) $I = 4$, $V = 4$ ✓

(iii) (a) 2Ω ✓

(v) (a) 1 ✓

4M

4.

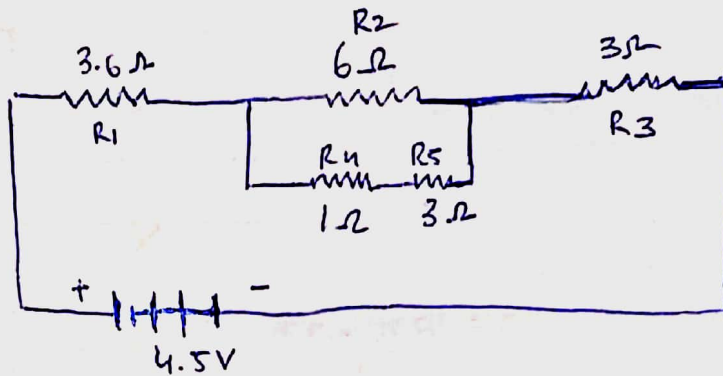

R_4 and R_5 are in series and both are parallel to R_2 .

$$\begin{aligned} \rightarrow R_B &= R_4 + R_5 \\ &= 1 + 3 \\ &= 4\Omega \end{aligned}$$

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{6} \Rightarrow R = \frac{4+6}{24} \Rightarrow \frac{10}{24}$$

$$R_p = \frac{24}{10} = 2.4\Omega$$

This effective R is in series with R_1 and R_3

$$\begin{aligned} \therefore R_S &= 3.6 + 2.4 + 3 \\ &= 9.0\Omega \end{aligned}$$

$$V = 4.5V$$

$$R = 9\Omega$$

$$I = \frac{V}{R}$$

$$\begin{array}{r} 3.6 \\ 2.4 \\ \hline 6.0 \\ 3.0 \\ \hline 9.0 \end{array}$$

$$= \frac{4.5}{9} \times 10$$

$$= \frac{45}{90} \Rightarrow \frac{1}{2} \Rightarrow \therefore I = 0.5 \text{ A}$$

\therefore the current passing is 0.5 A ✓ 3M

5. (a) R_4 and R_5 are in series connection. ✗

(b) R_3 and R_2 are in parallel connection. ✓

(c) R_1 will not contribute to the effective resistance. It is joined back to itself, therefore the resistance cancels out.

$$\frac{1}{R_p} = \frac{1}{R_3} + \frac{1}{R_2}$$

$$= \frac{1}{2} + \frac{1}{2} \Rightarrow 1$$

2M

$$\therefore R_p = 1 \Omega$$

$$R_s = R_4 + R_5 + 1$$

$$= 2 + 2 + 1$$

$$= \underline{\underline{5 \Omega}}$$

$$V = 5 \text{ V}$$

$$\therefore I = \frac{V}{R} \Rightarrow \frac{5}{5}$$

$$\therefore \underline{\underline{I = 1 \text{ A}}}$$

6. $P = 24 \text{ W}$

$$V = 12 \text{ V}$$

$$P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P} \Rightarrow \frac{12 \times 12}{24} \Rightarrow 6 \Omega$$

$$\therefore R = 6 \Omega$$

$$V = 6 \text{ V}$$

$$P = \frac{V^2}{R} \Rightarrow \frac{6 \times 6}{6} \Rightarrow \underline{\underline{6 \text{ W}}}$$

✓ 301

9. (a) We can place the switch in series with lamp L2 another switch, in series, with lamp L3. Since, this is a parallel connection, if we switch on/off L2 and L3, it will not affect L1. $\frac{1}{2}$

(b) The name is a parallel connection. ✓ (1)

(c) $V = 6V + 6V$

$= 12V$

$A_1 \rightarrow I = 1.5A$ ✓ $\frac{1}{2}$

\therefore total R of circuit = $\frac{V}{I}$ ($\because V = IR$) (Ohm's law)

$\Rightarrow \frac{12}{1.5} \Rightarrow \frac{4}{0.5} \times 10$

$\Rightarrow \frac{40}{5} \Rightarrow \underline{\underline{8\Omega}}$ ✗

A2 reading $\rightarrow V = 12V$

$R = 8\Omega$

$I = \frac{V}{R}$

$= \frac{12}{8} \Rightarrow \frac{6}{4} \Rightarrow \frac{2}{3}$

$\therefore I = 0.666A$

$= \underline{\underline{0.67A}}$ ✗


(d) $R = 8\Omega$

$I = 1.5A$

$V = IR$

$= 8 \times 1.5$

$= \underline{\underline{12V}}$

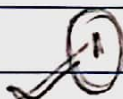

3/5M

4.5
x8
12.0